



MIDDLE EAST TECHNICAL UNIVERSITY
DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

EE463 – Term Project: AC to DC Motor Drive

Simulation Report

Group Power Quality

Alper Çakıroğlu
2276772

Mustafa Mert Sarıkaya
2094381

Fatih Serdar Sağlam
2481828

TABLE OF CONTENTS

ABSTRACT	3
INTRODUCTION & SPECIFICATIONS	3
TOPOLOGY SELECTION	4
<i>1a) Three-Phase Full-Bridge Diode Rectifier and Buck Converter</i>	<i>4</i>
<i>1b) Three-Phase Thyristor Rectifier</i>	<i>5</i>
<i>2) Decision & Design Considerations</i>	<i>6</i>
ANALYTICAL CALCULATIONS	7
COMPONENT SELECTION	8
SMD Bridge Rectifiers: Z4DGP406L-HF [1]	8
Buck-Capacitor: EEE-FP1V220AR [2]	8
Rectifier-Out Capacitor (DC Link Capacitor): UVZ2G221MRD [3]	9
Current Measurement Resistor: PE0603DRF570R01L [4]	9
Buck MOSFETs: FDT3N40TF [5]	9
Buck Inductor: 744822222 [6]	10
Controller: LM5117 [7]	11
SIMULATION RESULTS	11
Input Torque Waveform	12
Bridge Rectifier Output Voltage	12
Inductor Current Waveform	13
Mosfet Voltage Waveform	13
Buck Converter Voltage and Current Waveform	14
PCB DESIGN	15
CONCLUSION	20
REFERENCES	21

I. ABSTRACT

So as to present the preliminary design of EE463 Static Power Conversion course Term Project, we, the group of Power Quality, write this report of simulation. The purpose of the term project is to design an AC-DC motor drive in order to illuminate the street by the use of a wind turbine generator and a battery. Possible solution approaches are discussed in detail, simulation is performed to meet the requirements in Simulink environment, useful and proper components are selected considering vital parameters and PCB design is done to realize the product.

II. INTRODUCTION & SPECIFICATIONS

As the name of the course implies, the aim of static power conversion is to control and convert the electrical power by the use of power electronic components. Thus, one can produce conditioning power according to a specific application. In order to achieve this objective, the Power Quality does a hardware project of an AC to DC motor drive, which is conducted for EE463 course.

The steps of the project are as follows: Firstly, we decide on a suitable topology to meet the project requirements by comparing pros and cons of alternative solutions. Then, we analytically calculate the circuit parameters such as capacitor and inductor values, current and voltage ratings etc. In pursuit of analytical calculations, we select proper real components on the market. We also choose the control mechanism for our implementation. Component parameters, prices and volumes are considered important while the selection process. Then, we implement the simulation according to the selected design and components, and check if the project requirements are satisfied or not. Lastly, the PCM of the circuit is designed in order to realize the system as a hardware project.

We are asked to regulate the incoming power to feed both load and the battery. Since the wind speed is changing in time, a controlled AC to DC converter circuit with the following requirements should be performed:

- **Open circuit voltage peak:** $330\text{ V}_{\text{line-to-line}}$
- **Battery capacity:** 13 Ah
- **Battery nominal voltage:** 24 V
- **Output current:** 2 A
- **Output current ripple:** %20 of average current
- **Inertia:** 0.00027 kg.m^2
- **Viscous Damping:** 0.005024 N.m.s
- **Poles:** 2
- **Voltage Constant:** 110 Vpeak-l/krpm
- **Stator Resistance:** 10.58 Ohm
- **Armature Inductance:** 16.7 mH

III. TOPOLOGY SELECTION

The basis of the project is firstly to choose a proper converter topology to use by comparing pros and cons of various solution choices. We should take into account the parameters of efficiency, cost and design complexity. In our case, the practical implementations on the market limits our options by two, as the exemplification in the term project description implies:

- a. Diode Rectifier and Buck Converter
- b. Three-Phase Thyristor Rectifier

The principles of operation for given topologies are explained in different sections to compare them with an analytical focus:

1a) Three-Phase Full-Bridge Diode Rectifier and Buck Converter

As a rectifier, in “Diode Rectifier and Buck Converter” topology, we have two universal bridges at the input side, each has two bridge arms. Then, we have a rectifier capacitor at the outputs of the bridges. The duty cycle of the generated signal changes with respect to the output of the wind turbine machine that is somehow proportional with the wind speed.

Then, we have a buck converter for lowering the DC output of the rectifier by a switching tool of MOSFET and a capacitor and inductor in series at the output of the converter. The rectifier part of the topology is shown in the following figure.

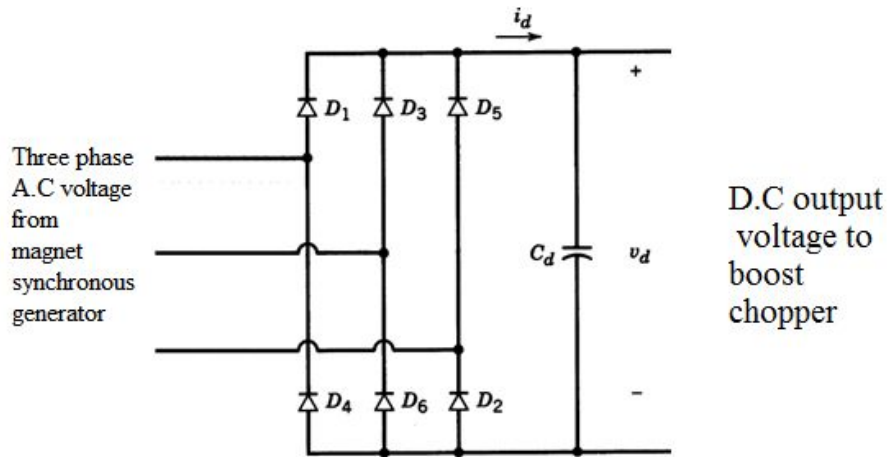


Figure 1: Circuit of diode rectifier (3 phase)

There should be a control mechanism for the determination of the switching frequency of MOSFET. This is performed by a pulse width modulation (PWM) signal applied to the gate input of the MOSFET, coming from a controller, either analog or a microcontroller.

The amplitude of the PWM signal does not exceed 5V. The PWM circuit is needed to be isolated from the main power side of high voltage. Therefore, isolation components should be also added to the circuitry.

We may list the pros and cons of “Diode Rectifier and Buck Converter” topology as follows:

1. Pros

- a. *i. Output ripples can be controlled by the output L filter.*
- b. *The switching frequency can be controlled easily.*
- c. *The efficiency is relatively high.*

2. Cons

- a. *The losses may be high when high frequency switching is used.*
- b. *The complexity is relatively high, by means of the number of components.*
- c. *The cost may be high as a result of part b.*
- d. *One should consider the discontinuous conduction mode of the converter.*

1b) Three-Phase Thyristor Rectifier

The “Three-Phase Thyristor Rectifier” topology requires six thyristors. For each gate of the thyristors, PWM signals with 120 degrees of phase shift are needed. Firing angle is arranged to meet the output voltage requirement.

The circuit of “Three-Phase Thyristor Rectifier” topology can be seen in the following figure. To play with the average output voltage, there should be a control circuitry for gate signals and firing angles.

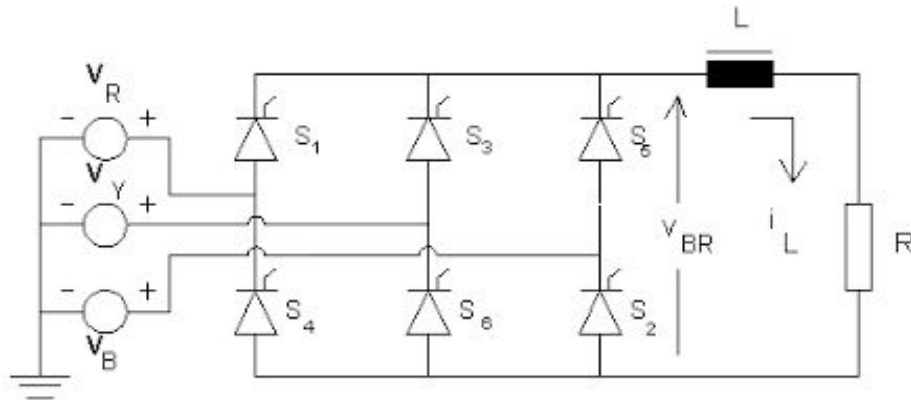


Figure 2: Circuit of full bridge thyristor rectifier (3 phase)

The most attractive part of this topology is to achieve desired negligible ripple without any buck/boost converter or capacitor in the DC side. The vital disadvantage of this topology is some kind of synchronization problem. The controller has to be in phase with the AC input part and this requirement makes the controller much more complex with respect to the previous one. In addition, the resulting power factor is smaller for low voltage levels because of the delay presented in the firing angle.

We may list the pros and cons of “Three-Phase Thyristor Rectifier” topology as follows:

1. Pros

- a. Output ripples are lower.*
- b. No need for output LC filtering.*
- c. Output voltage is relatively high.*
- d. The efficiency is relatively high.*

2. Cons

- a. Need for a much complicated control circuit for synchronization.*
- b. Low power and discrete power factor.*

2) Decision & Design Considerations

The “Power Quality” group decides upon the topology of “Diode Rectifier and Buck Converter for the following reasons:

- The available components in the market are much more diverse.
- The frequency range is much broader. So the output ripple can be adjusted more precisely.
- Relatively cheap if we sacrifice from the low output ripple.
- For high duty cycle values, which may be the case in our project, it is more efficient.

IV. ANALYTICAL CALCULATIONS

The analytical calculations of the circuit begin with the simple analysis of the buck converter. At first, the duty cycle that needed to operate the converter is calculated. It's seen that with the variation of input voltage, the duty cycle also changes in specific range.

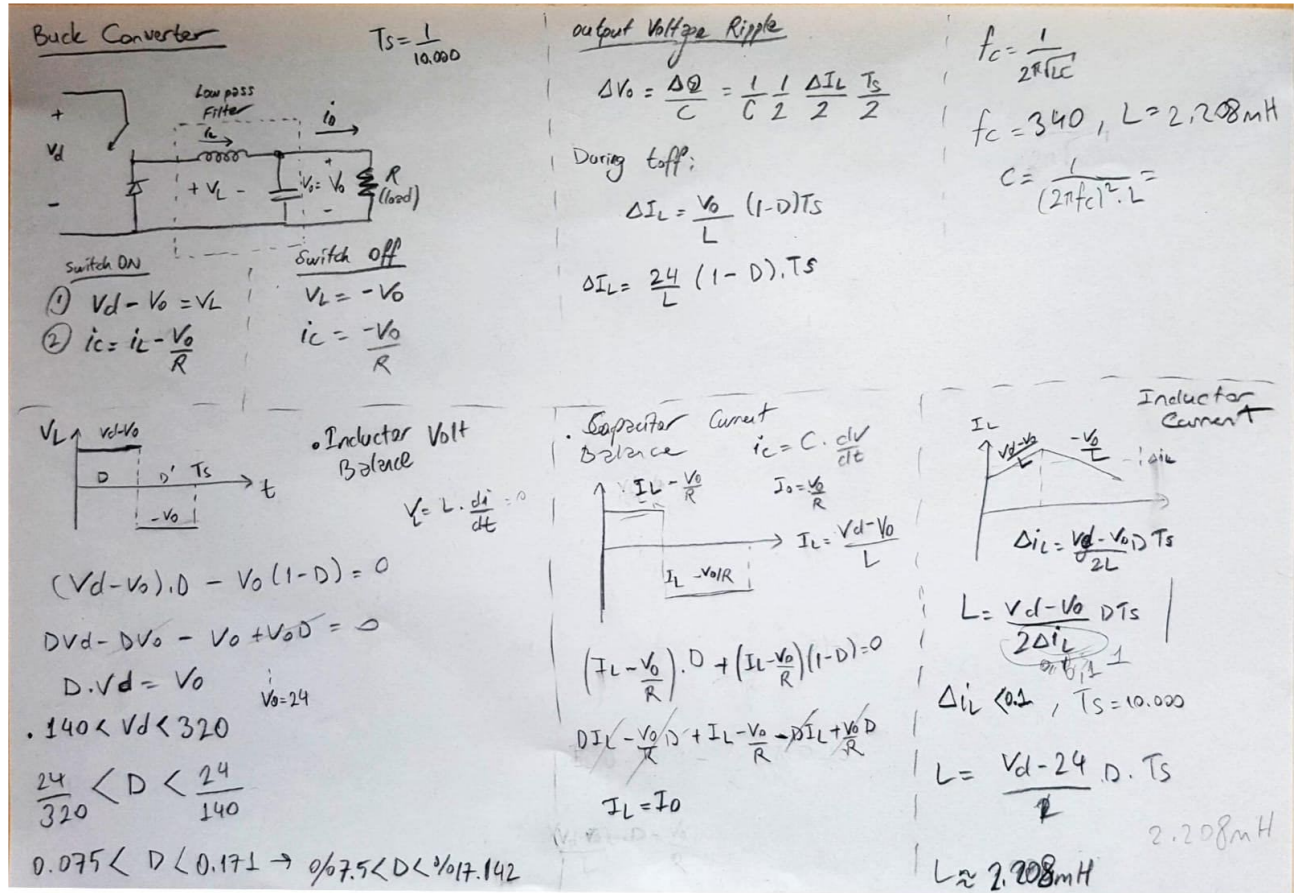


Figure 3: Initial analysis of buck converter

After initial analysis, the inductor and capacitance value of the circuit is calculated in MATLAB as given below.

```
Vout = 24;
Vin = 300; %It will be in a range e.g. 150 to 330V
i_out = 2;
fs = 50000; %switching frequency
fc = 339; %Corner frequency for LC filter
delta_i = 0.2*i_out; %Desired inductor ripple current

delta_Vo = 0.05; %Desired peak to peak output voltage

D = Vout/Vin; %Duty cycle will also be in a range due to Vin variance

L = Vout*(1-D)/(fs*delta_i); %Inductor sizing

C = 1/(((2*pi*fc)^2)*L); %Capacitor sizing related to corner frequency
% C = delta_i/(8*fs*delta_Vo); %Capacitor sizing

Diode_size = i_out*(1-D); %V30K45, shotky
```

V. COMPONENT SELECTION

We selected the components of rectifiers, capacitors, inductors, resistors and MOSFETs as follows:

1) SMD Bridge Rectifiers: Z4DGP406L-HF [1]

The specification of the bridge rectifiers is shown in the table below. The price of this component is 1.03USD. We use 2 of them. Total price is 2.06USD.

Parameter	Symbol	Z4DGP406L-HF				Unit
Repetitive Peak Reverse Voltage	V_{RRM}	600				V
Average Forward Current	$I_{(AV)}$	4.0				A
Peak Forward Surge Current, 8.3ms single half sine-wave, superimposed on rated load (JEDEC Method)	I_{FSM}	150				A
Operating Junction Temperature Range	T_J	-55 to +175				°C
Storage Temperature Range	T_{STG}	-55 to +175				°C
Parameter	Symbol	Conditions	Min.	Typ.	Max.	Unit
Forward Voltage	V_F	$I_F = 2.0A$ $I_F = 4.0A$	- -	0.86 0.90	0.90 0.95	V
Repetitive peak reverse current	I_{RRM}	$V_R = \text{Max. } V_{RRM}, T_a = 25^\circ\text{C}$	-	0.08	5	μA
Current squared time	I^2t	$t < 8.3\text{ms}, T_a = 25^\circ\text{C}$	-	93.38	-	A^2S
Junction capacitance	C_J	$V_R = 4V, f = 1.0\text{MHz}$	-	45	-	pF
Thermal resistance	$R_{\theta JA}$	Junction to ambient (Note)	-	35	-	°C/W
	$R_{\theta JL}$	Junction to lead	-	15	-	°C/W
	$R_{\theta JC}$	Junction to case	-	10	-	°C/W

Table 1: The Technical Specification of the Bridge Rectifier

2) Buck-Capacitor: EEE-FP1V220AR [2]

The specification of the buck capacitor is shown in the table below. The price of this component is 0.43USD. We use 1 of them. Total price is 0.43USD.

Body shape	Surface mount type (vertical mount style)
Polarity type	Polar
Rated voltage (V)	35
Capacitance (μF)	22
Tolerance on capacitance (%)	-40
Tangent of loss angle (max.)	0.12
Leakage current (max.) (μA)	7.Tem
Category temperature range (°C)	-160

Table 2: The Technical Specification of the Buck Capacitor

3) Rectifier-Out Capacitor (DC Link Capacitor): UVZ2G221MRD [3]

The specification of the DC link capacitor is shown in the table below. The price of this component is 4.23USD. We use 1 of them. Total price is 4.23USD.

Tolerance	$\pm 20\%$
Lifetime @ Temp.	1000 Hrs @ 105°C
Operating Temperature	-40°C ~ 105°C
Capacitance	220 μ F
Voltage - Rated	400V
Ripple Current @ Low Frequency	660mA @ 120Hz
Ripple Current @ High Frequency	1.056A @ 10kHz

Table 3: The Technical Specification of the Rectifier-Out Capacitor

4) Current Measurement Resistor: PE0603DRF570R01L [4]

The specification of the current measurement resistor is shown in the table below. The price of this component is 0.07USD. We use 1 of them. Total price is 0.07USD

TYPE	DESCRIPTION
Tolerance	$\pm 0.5\%$
Power (Watts)	0.5W, 1/2W
Composition	Metal Foil
Temperature Coefficient	$\pm 100\text{ppm}/^\circ\text{C}$
Operating Temperature	-55°C ~ 170°C
Resistance	10 mOhms

Table 4: The Technical Specification of the Current Measurement Resistor

5) Buck MOSFETs: FDT3N40TF [5]

The specification of the buck MOSFETs is shown in the table below. The price of this component is 0.65USD. We use 2 of them. Total price is 1.30USD.

Technology:	Si
Transistor Polarity:	N-Channel
Number of Channels:	1 Channel
V _{ds} - Drain-Source Breakdown Voltage:	400 V
I _d - Continuous Drain Current:	2 A
R _{ds On} - Drain-Source Resistance:	2.8 Ohms
V _{gs} - Gate-Source Voltage:	- 30 V, + 30 V
V _{gs th} - Gate-Source Threshold Voltage:	5 V
Q _g - Gate Charge:	4.5 nC
Minimum Operating Temperature:	- 55 C
Maximum Operating Temperature:	+ 150 C
P _d - Power Dissipation:	2 W
Channel Mode:	Enhancement
Fall Time:	25 ns
Rise Time:	30 ns
Typical Turn-Off and On Delay Time:	10 ns

Table 5: The Technical Specification of the Buck MOSFETs

6) Buck Inductor: 744822222 [6]

The specification of the buck inductor is shown in the table below. The price of this component is 4.43USD. We use 1 of them. Total price is 4.43USD

Inductance:	2.2 mH
Tolerance:	30%
Maximum DC Current:	2:00 OO
Maximum DC Resistance:	70 mOhms
Minimum Operating Temperature:	- 40 C
Maximum Operating Temperature:	+ 125 C

Table 6: The Technical Specification of the Buck Inductor

7) Controller: LM5117 [7]

The specification of the controller is explained in the PCB Design section and its total price is 6USD.

The **total cost** of the components is:

$$(1.03 \times 2 + 0.43 \times 1 + 4.23 \times 1 + 0.07 \times 1 + 0.65 \times 2 + 4.43 \times 1 + 6 \times 1) \text{ USD} = \mathbf{18.52 \text{ USD}}$$

VI. SIMULATION RESULTS

The simulation is performed on Matlab Simulink environment by implementing the components and the controller that have been selected in the previous part. The schematic is:

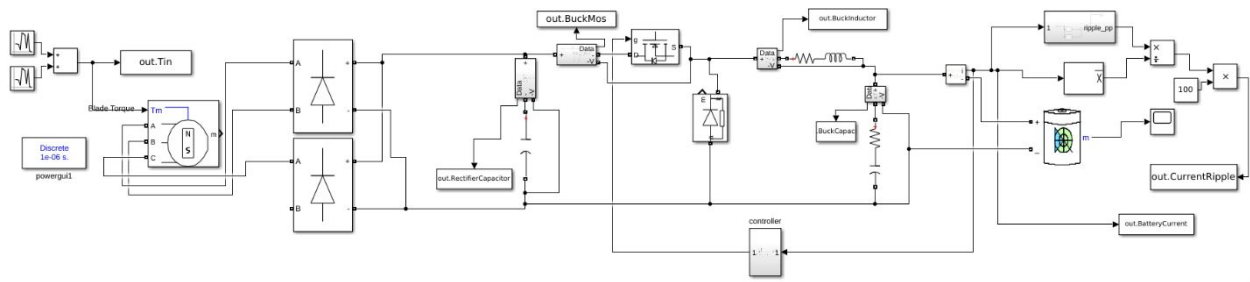


Figure 4: Diode Rectifier and Buck Converter Schematic

The controller part of the circuit is shown below:

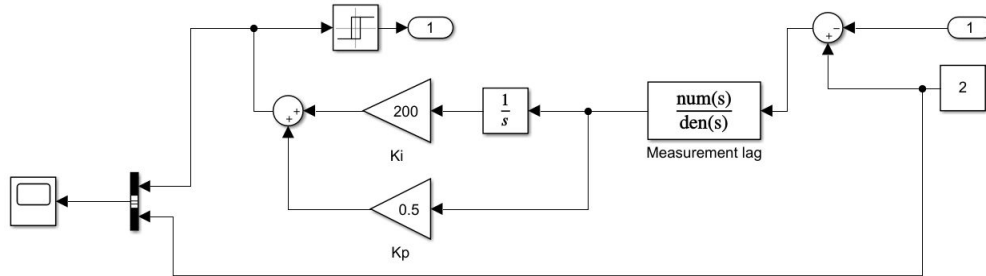


Figure 5: The Controller Subsystem Schematic

The simulation includes following components: A Permanent Magnet Synchronous Machine represents the wind turbine generator. The wind is represented by the sum of two normally distributed random numbers that generates torque on the turbine. Then, the resulting phases of the machine are connected to the inputs of the full bridge rectifiers that are represented by universal bridges on simulation. We have a lead-acid battery to store energy from the machine and supply energy to the system. The negative side of the output of the bridge is directly connected to the negative side of the battery. In order to achieve buck conversion, a MOSFET is inserted for the purpose of switching. The drain input of the MOSFET is connected to the positive output of the bridge. So as to achieve the desired output current, the gate signal of MOSFET is fed by an analog hysteresis feedback control with K_p value of 0.5 and K_i value of 200. The control system is fed by an external voltage. As smoothing components, we also add the required filtering elements such as a buck capacitor and inductor, a rectifier-out capacitor.

1) Input Torque Waveform

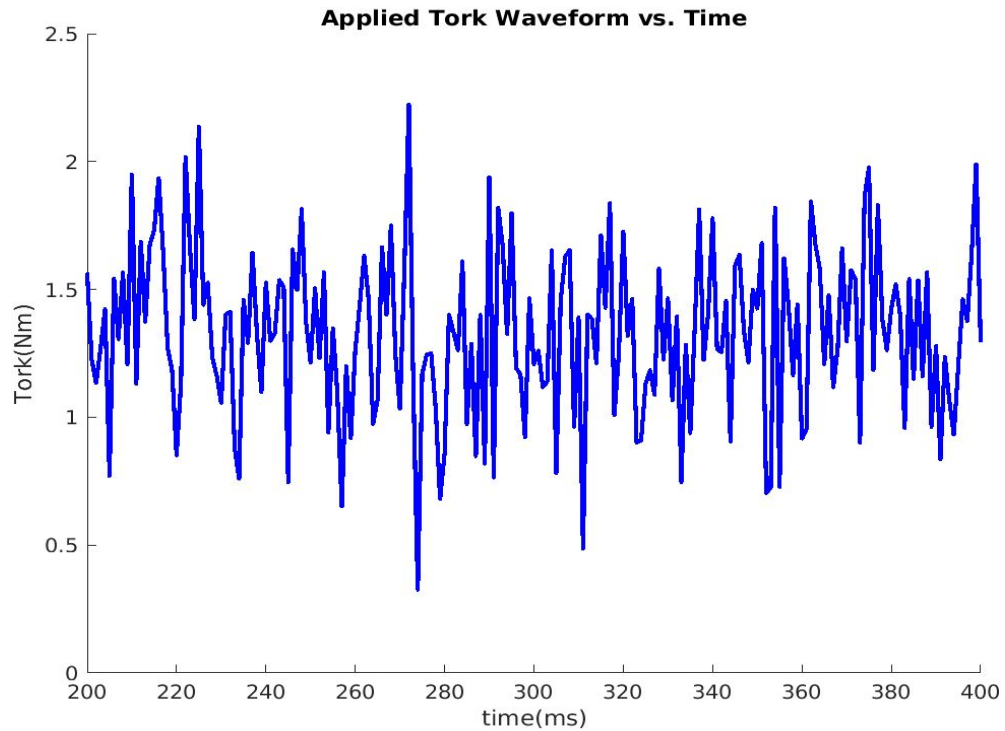


Figure 6: Random input for wind turbine generator

Wind turbine is not exposed to fixed power, its mechanical input changing with air conditioning. As seen in the figure, random input applied for our design to see our device's quality in changing voltage level.

2) Bridge Rectifier Output Voltage

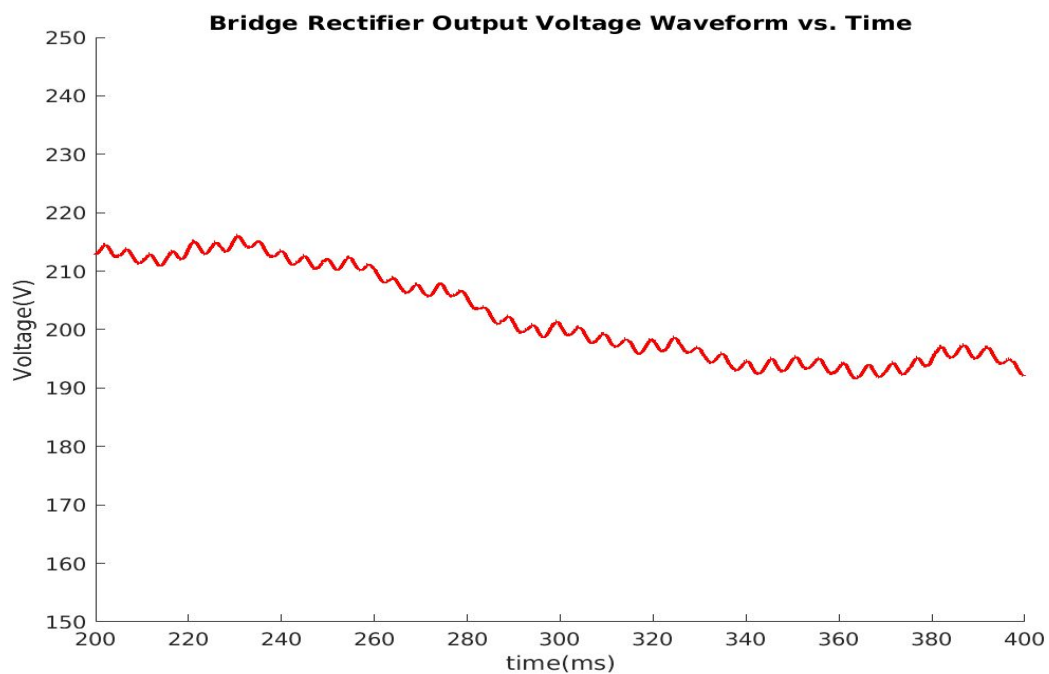


Figure 7: 3 Phase Bridge Diode Rectifier Output Waveform

After rectification of varying input voltage, the dc voltage is obtained on the dc link capacitor. This voltage still varies between 190 to 220V. The buck converter side of the circuit is needed to implement to have constant current at the output. To achieve that, the duty cycle of the buck's mosfet should be arranged with the selected controller.

3) Inductor Current Waveform

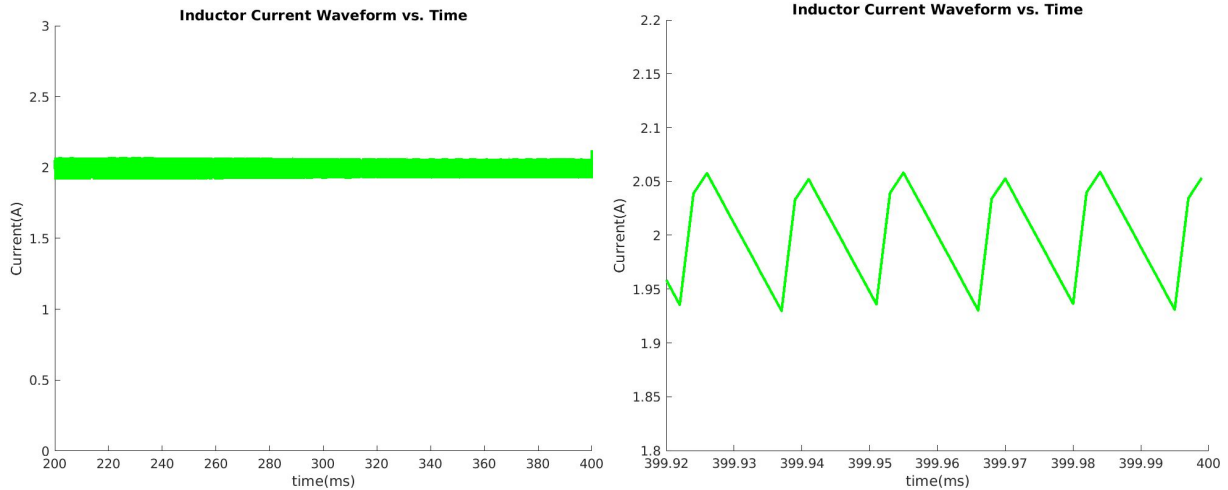


Figure 8: Inductor Current Waveform

We have low voltage ripple so filter capacitor current is small and inductor current close to the output current. Our model has a 2.2mH inductance for step down voltage from 300 V to 24 V so it has a small duty cycle and current increase faster than current decrease. Its ripple is smaller than 400mA when changing input voltage applied.

4) Mosfet Voltage Waveform

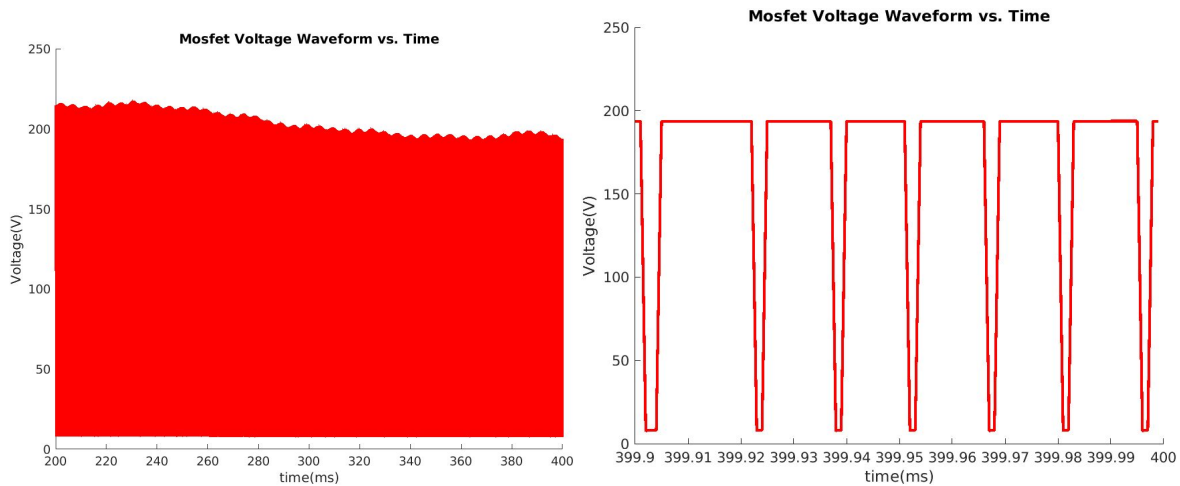


Figure 9: Buck Converter switching Mosfet Waveform

Mosfet voltage equal to bridge rectifier output when it is off as seen in figures. When control signal applied mosfet operates in saturation region and its voltage reduces to V_f .

5) Buck Converter Voltage and Current Waveform

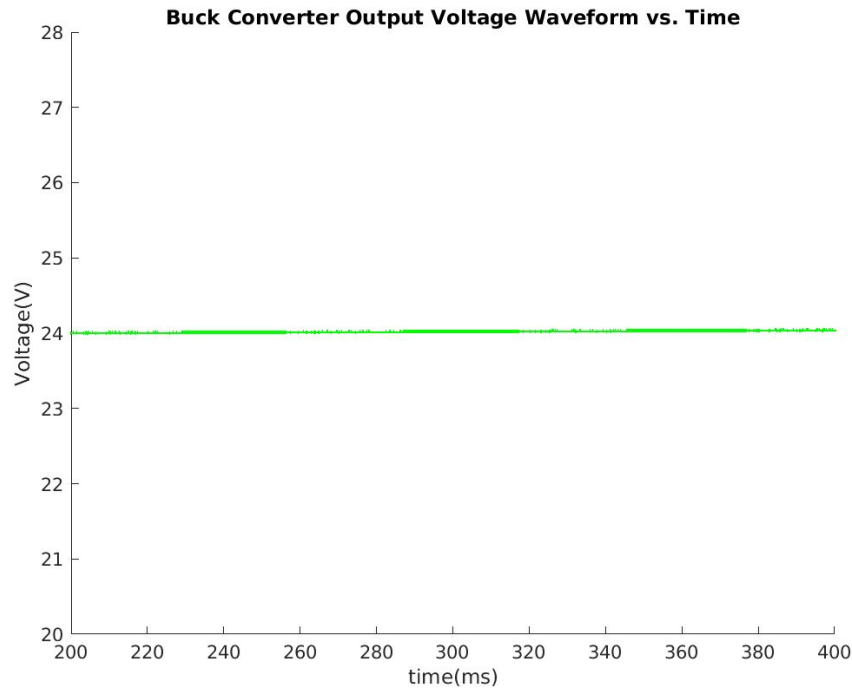


Figure 10: Buck Converter Output Voltage Waveform

Since our buck converters output voltage directly connected to the battery, output voltage level is so close to battery nominal voltage and it does not have high voltage ripple as seen in the figure.

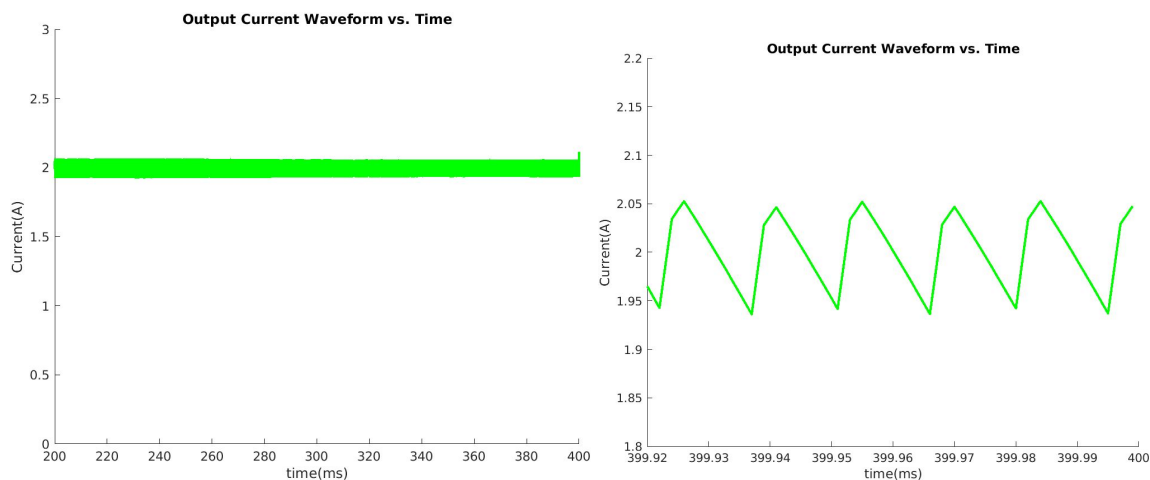


Figure 11: Buck Converter Output Current Waveform

One of the important conditions for this term project is to keep current ripple lower than %20 of average current. As seen in the figure output current ripple is around 100mA which is the desired value for the designed circuit.

VII. PCB DESIGN

The simulated circuit for the term project is implemented on Altium Designer. The selected components are implemented in the Altium library. The schematics of the circuit is given in this section. However, while the circuit is implemented, we encountered undesired problems. The controller couldn't be implemented completely. Moreover, rectifier diodes' footprints are also missing for this part. Because of that, the PCB design for the project could not be completed.

In simulation, the control method of the circuit is held by the PI controller. For real application, we use an IC controller to have constant current at the output. To do so, LM5117 controller is selected.

To use LM5117, detail specification for each connection of IC is calculated according to application notes of the component. As "Power Quality" group, we still have struggles about the controller whether it is selected correctly or not. Because of that, a typical application for constant current and voltage regulation, pin functions, and absolute ratings are given to have better understanding on the device.

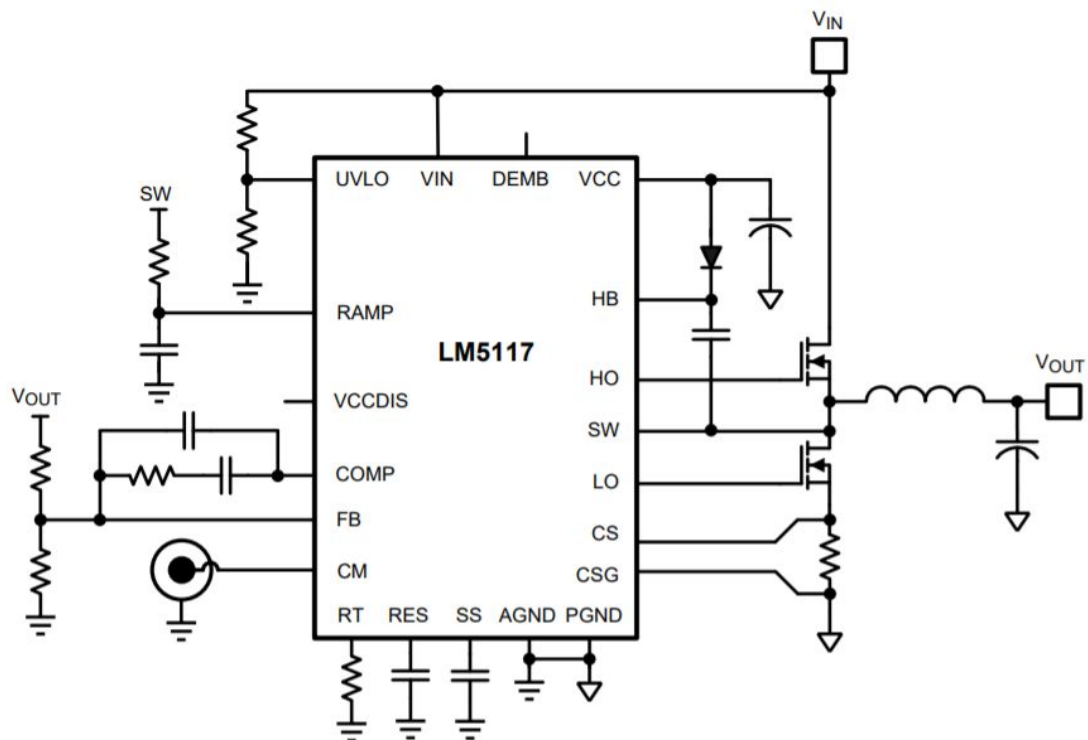


Figure 12: Typical application of LM5117

The typical application is given to understand the implementation of LM5117. In application notes of TI, the controller can be used for constant current and constant voltage method. In the figure below, the current and voltage control method is given for output current as 2A and output voltage as 5V. For our application, the calculations are trying to be done for 2A output current and 24V output voltage.



The pin functions of the controller:

PIN			TYPE ⁽¹⁾	DESCRIPTION
HTSSOP	WQFN	NAME		
1	24	UVLO	I	Undervoltage lockout programming pin. If the UVLO pin voltage is below 0.4 V, the regulator is in the shutdown mode with all functions disabled. If the UVLO pin voltage is greater than 0.4 V and less than 1.25 V, the regulator is in standby mode with the VCC regulator operational, the SS pin grounded, and no switching at the HO and LO outputs. If the UVLO pin voltage is above 1.25 V, the SS pin is allowed to ramp and pulse width modulated gate drive signals are delivered to the HO and LO pins. A 20µA current source is enabled when UVLO exceeds 1.25 V and flows through the external UVLO resistors to provide hysteresis.
2	1	DEMB	I	Optional logic input that enables diode emulation when in the low state. In diode emulation mode, the low-side NMOS is latched off for the remainder of the PWM cycle after detecting reverse current flow (current flow from output to ground through the low-side NMOS). When DEMB is high, diode emulation is disabled allowing current to flow in either direction through the low-side NMOS. A 50-kΩ pull-down resistor internal to the LM5117 holds DEMB pin low and enables diode emulation if the pin is left floating.
3	2	RES	O	The restart timer pin that configures the hiccup mode current limiting. A capacitor on the RES pin determines the time the controller remains off before automatically restarting. The hiccup mode commences when the controller experiences 256 consecutive PWM cycles of cycle-by-cycle current limiting. After this occurs, a 10-µA current source charges the RES pin capacitor to the 1.25 V threshold and restarts LM5117.
4	3	SS	I	An external capacitor and an internal 10-µA current source set the ramp rate of the error amplifier reference during soft-start. The SS pin is held low when VCC < 5 V, UVLO < 1.25 V or during thermal shutdown.
5	4	RT	I	The internal oscillator is programmed with a single resistor between RT and the AGND. The recommended maximum oscillator frequency is 750kHz. The internal oscillator can be synchronized to an external clock by coupling a positive pulse into the RT pin through a small coupling capacitor.
6	5	AGND	G	Analog ground. Return for the internal 0.8 V voltage reference and analog circuits.
7	7	VCCDIS	I	Optional input that disables the internal VCC regulator. If VCCDIS > 1.25 V, the internal VCC regulator is disabled. VCCDIS has an internal 500-kΩ pulldown resistor to enable the VCC regulator when the pin is left floating. The internal 500-kΩ pull-down resistor can be overridden by pulling VCCDIS above 1.25 V with a resistor divider connected to an external bias supply.
8	8	FB	I	Feedback. Inverting input of the internal error amplifier. A resistor divider from the output to this pin sets the output voltage level. The regulation threshold at the FB pin is 0.8 V.
9	9	COMP	O	Output of the internal error amplifier. The loop compensation network should be connected between this pin and the FB pin.
10	10	CM	O	Current monitor output. Average of the sensed inductor current is provided. Monitor directly between CM and AGND. CM should be left floating when the pin is not used.
11	11	RAMP	I	PWM ramp signal. An external resistor and capacitor connected between the SW pin, the RAMP pin and the AGND pin sets the PWM ramp slope. Proper selection of component values produces a RAMP signal that emulates the AC component of the inductor with a slope proportional to input supply voltage.
12	12	CS	I	Current sense amplifier input. Connect to the high-side of the current sense resistor.
13	13	CSG	G	Kelvin ground connection to the current sense resistor. Connect directly to the low-side of the current sense resistor.
14	14	PGND	O	Power ground return pin for low-side NMOS gate driver. Connect directly to the low-side of the current sense resistor.
15	15	LO	P/O/I	Low-side NMOS gate drive output. Connect to the gate of the low-side synchronous NMOS transistor through a short, low inductance path.
16	16	VCC	I/O	Bias supply pin. Locally decouple to PGND using a low ESR/ESL capacitor located as close to controller as possible.
17	18	SW	O	Switching node of the buck regulator. Connect to the bootstrap capacitor, the source terminal of the high-side NMOS transistor and the drain terminal of the low-side NMOS through a short, low inductance path.

Figure 14: Pin functions of LM5117

	MIN	MAX	UNIT
VIN to AGND	-0.3	75	V
SW to AGND	-3.0	75	V
HB to SW	-0.3	15	V
VCC to AGND ⁽²⁾	-0.3	15	V
HO to SW	-0.3	HB + 0.3	V
LO to AGND	-0.3	VCC + 0.3	V
FB, DEMB, RES, VCCDIS, UVLO to AGND	-0.3	15	V
CM, COMP to AGND ⁽³⁾	-0.3	7	V
SS, RAMP, RT to AGND	-0.3	7	V
CS, CSG, PGND, to AGND	-0.3	0.3	V
Storage Temperature, T _{stg}	-55	150	°C
Junction temperature	-40	150	°C

Figure 15: Absolute ratings of LM5117

Detailed Design Procedure for LM5117 is:

Design Parameter	Example Value
Output Voltage	24V
Full load current, I _{out}	2A
Minumum input voltage, V _{in} (min)	12V considered / not sure
Maximum input voltage, V _{in} (max)	24V considered / not sure
Switching frequency, f _{sw}	100kHz
Diode emulation	yes
External VCC Supply	yes / 12V considered

Figure 16: Detailed Design Procedure for LM5117

From the application notes of the controller, desired parameters are taken. For this controller, there is too much to consider selecting the components. Because we are not sure to continue with this controller, the circuit is only implemented according to application values. However, these considerations are tried to be held to have an understanding of the controller.

After trying to select desired parameters for the controller, the circuit is built in Altium schematics. The footprint of each selected component is implemented in the Altium library. The circuit has three parts;

- Rectifier circuit
- Buck Converter
- Current Control

In the rectifier circuit, the rectifier diodes and dc link capacitor are implemented. Input of this circuit is taken by a 4 pos pluggable terminal. This terminal is considered to get input voltage from synchron machine.

In the buck converter schematic, the controller and the buck converter is built. Different from simulation of the project, two synchron MOSFET is used. Implementation of the controller is not fully completed.

In the current control schematic, the logic to have constant current is tried to be applied. We still have struggles about to have the exact values of resistive and capacitive elements for this method.

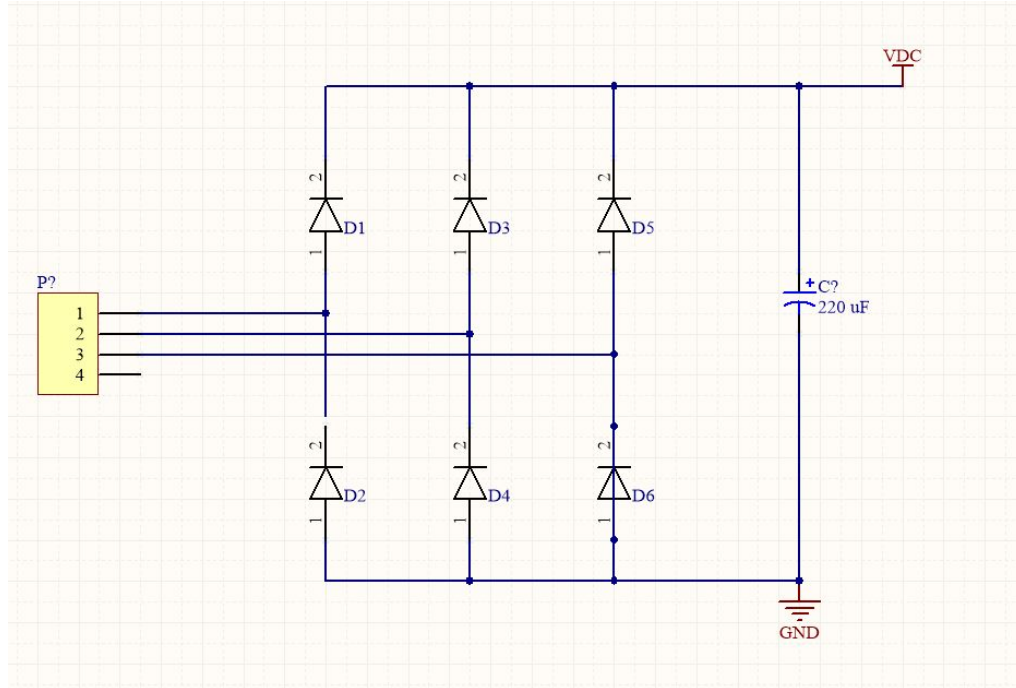


Figure 17 : Rectifier circuit schematic

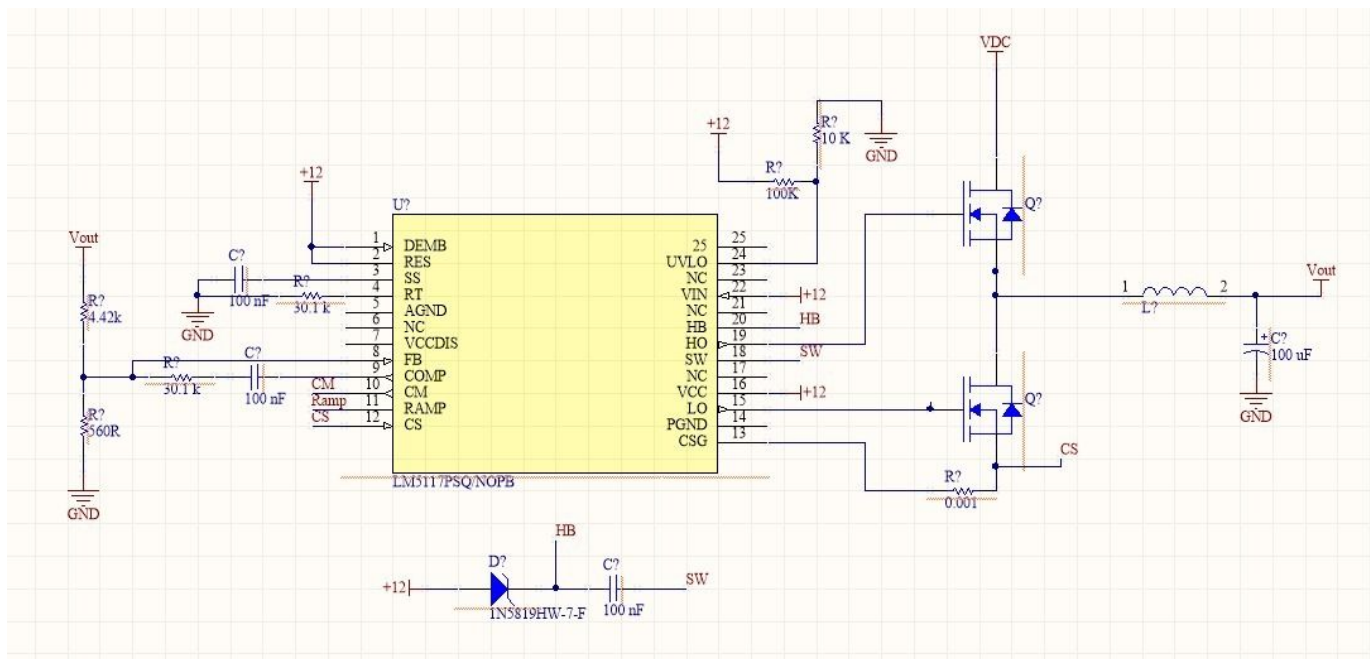


Figure 18: Buck Converter Schematic

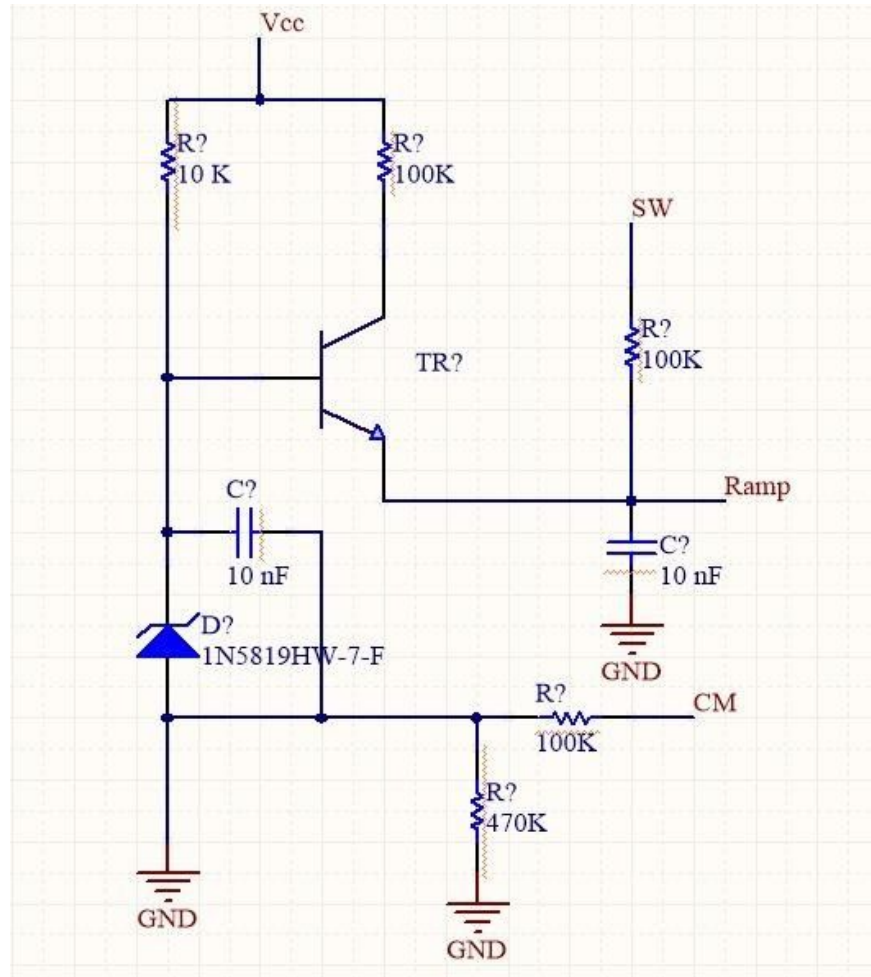


Figure 19: Current Control Schematic

As it mentioned, the pcb design of the circuit couldn't be finished. Problems encountered while trying to update schematic to pcb is given below.

To be handled;

- Selection of the controller should be done according to given feedback.
- Power ports should communicate between sheets.
- Compile problems should be understood.
- Missing footprint of 400V rectifier diodes should be added.

VIII.CONCLUSION

For the project to regulate the incoming power from the wind turbine generator to feed the battery, a three-phase full-bridge diode rectifier and buck converter circuit is implemented. Analytical calculations of the circuit are measured and its simulations are analyzed in the MATLAB environment. Along with the calculations and simulation, the needed materials are selected in the market. After these progress, the project is tried to implement for real life application. Its schematics are created in Altium Designer. For the pcb design, the project team encountered difficulties to be handled.

IX. REFERENCES

- [1]<https://www.digikey.com/en/products/detail/comchip-technology/Z4DGP406L-HF/4386624>
- [2]<https://www.digikey.com/en/products/detail/panasonic-electronic-components/EEE-FP1V220AR/1701004>
- [3]<https://www.digikey.com/en/products/detail/nichicon/UVZ2G221MRD/589194>
- [4]<https://www.digikey.com/en/products/detail/yageo/PE0603DRF570R01L/5913781>
- [5]<https://www.mouser.com.tr/ProductDetail/ON-Semiconductor-Fairchild/FDT3N40TF/?qs=%2Fha2pyFaduiyEk53MxufExrnikJu3q6flJ%252B5sv%2FExVw%3D>
- [6]<https://www.mouser.com.tr/ProductDetail/Wurth-Elektronik/744822222/?qs=sGAepiMZZMv126LJFLh8yyIZIOICTdvmT6YHDAzFjvY%3D>
- [7]<https://www.ti.com/lit/ds/symlink/lm5117.pdf?ts=1608837436095>